

# Digital Engineering Project Task 1

Y3890959  
Y3878784

28th February 2023

# Task 1: Clock management through enable signals

## 1 - FSM Description

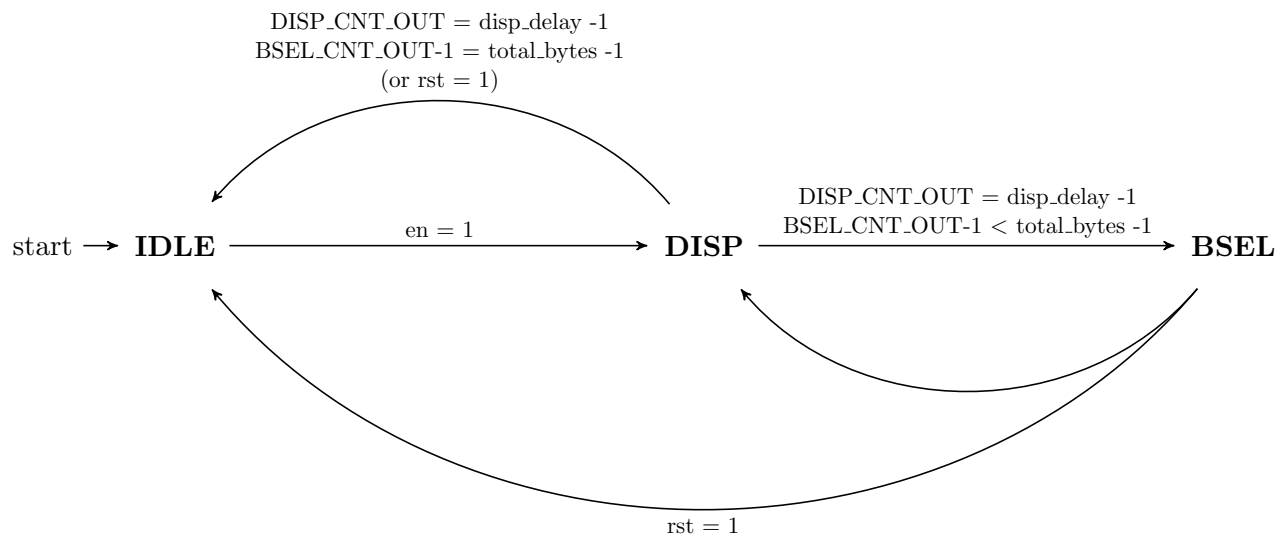


Figure 1: FSM state graph

Abbreviations: `DISP_CNT` - the counter that adds a delay to the LED display output. `BSEL_CNT` - the counter that increments for BSEL (byte select) so the correct byte can be displayed.

The FSM starts at **IDLE** state, where 'EN\_SOURCE' is low, all internal counters (**BSEL** and **DISP**) are reset and the LED array is off. When the 'en' pushbutton is toggled, the **DISP** state is entered. Entering this state after **IDLE**, the counters will be at 0, therefore 'EN\_SOURCE' will be set high, then low as soon as either of the counters start incrementing. This will trigger 'DATA\_SOURCE' to compute the next value which will be displayed. The **DISP** counter will start incrementing to add a delay for the LED display, once the counter reaches a maximum and the **BSEL** counter hasn't yet reached a maximum, the **BSEL** state will be set. Otherwise, the FSM goes back to the **IDLE** state as all bytes have been displayed with the delay. In the **BSEL** state, the **DISP** counter is reset and disabled, and the **BSEL** counter is enabled for an increment. Going back to **DISP** state will reset the **BSEL** counter. When the 'rst' button is toggled at any point, the logic must reset to **IDLE**.

STATE	EN_SOURCE	DISP_CNT_EN	DISP_CNT_RST	BSEL_CNT_EN	BSEL_CNT_RST	LED_DISPLAY				
IDLE	0	0	1	0	1	00000000				
DISP	1 when DISP_CNT_OUT and DISP_CNT_OUT = 0	1	0	0	0	SOURCE_DATA[7:0] when DISP_CNT_OUT is 0				
						SOURCE_DATA[15:8] when DISP_CNT_OUT is 1				
	0 otherwise					SOURCE_DATA[23:16] when DISP_CNT_OUT is 2				
						SOURCE_DATA[31:24] when DISP_CNT_OUT is 3				
BSEL	0	0	1	1	0	00000000				

Table 1: FSM table of outputs

## 2 - VHDL Code for 'STUDENT\_AREA'

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;
use work.DigEng.all;

-- This is where your work goes. Of course, you will have to put
-- your own comments in, to describe your work.

entity STUDENT_AREA is
  Generic (
    disp_delay : natural := 100000000;
    total_bytes : natural := 4
  );
  Port ( CLK_100MHZ : in  STD_LOGIC;
         -- Debounced button inputs (4=U, 3=C, 2=R, 1=L, 0=D)
         USER_PB : in  STD_LOGIC_VECTOR (4 downto 0);
         -- Board switches (not debounced)
         SWITCHES : in  STD_LOGIC_VECTOR (7 downto 0);
         -- Board LEDs
         LED_DISPLAY : out STD_LOGIC_VECTOR (7 downto 0);
         -- Control signals for the data source
         RST_SOURCE : out STD_LOGIC;
         EN_SOURCE : out STD_LOGIC;
         SOURCE_DATA : in  STD_LOGIC_VECTOR (31 downto 0)
       );
end STUDENT_AREA;

architecture Behavioral of STUDENT_AREA is

  signal EN, RST, CLK : STD_LOGIC;
  type state_type is (IDLE, DISP, BSEL); -- The FSM states
  signal state, next_state: state_type; -- The states as signals

  -- Internal signals for the counters enable and resets
  signal DISP_CNT_OUT : UNSIGNED (log2(disp_delay)-1 downto 0);
  signal BSEL_CNT_OUT : UNSIGNED (log2(total_bytes)-1 downto 0);
  signal DISP_CNT_EN, BSEL_CNT_EN, DISP_CNT_RST, BSEL_CNT_RST : STD_LOGIC;

begin

  RST <= USER_PB(1);
  EN <= USER_PB(3);
  CLK <= CLK_100MHZ;
  RST_SOURCE <= RST;

  -- Sets the state as IDLE (reset state) when the reset input is set high.
  -- At each clock cycle if the reset isn't high, the state is set to the next
  -- state.
  state_assignment : process (clk) is
  begin
    if rising_edge(clk) then
      if (rst = '1') then
        state <= IDLE;
      else
        state <= next_state;
      end if;
    end if;
  end process state_assignment;

```

```

-- Port map for the display delay counter
DISP_CNT: entity work.parameterizable_counter
GENERIC MAP (LIMIT => disp_delay)
PORT MAP(
    clk => clk,
    rst => DISP_CNT_RST,
    enable => DISP_CNT_EN,
    count_out => DISP_CNT_OUT
);

-- Port map for the byte select counter
BSEL_CNT: entity work.parameterizable_counter
GENERIC MAP (LIMIT => total_bytes)
PORT MAP(
    clk => clk,
    rst => BSEL_CNT_RST,
    enable => BSEL_CNT_EN,
    count_out => BSEL_CNT_OUT
);

fsm_process : process (state, en, rst, DISP_CNT_OUT, BSEL_CNT_OUT)
begin
    case state is
        when IDLE =>
            if en = '1' then
                next_state <= DISP;
            end if;
        when DISP =>
            -- When all of the bytes has been displayed and the delay has been completed,
            -- we can go back to the IDLE state to wait for the next enable signal.
            if ((DISP_CNT_OUT = disp_delay-1 and BSEL_CNT_OUT = total_bytes - 1) or rst = '1') then
                next_state <= IDLE;
            -- If the display delay has completed but there are still more bytes to be
            -- displayed, the next state can be set to BSEL (byte select), where the
            -- BSEL counter is incremented.
            elsif (DISP_CNT_OUT = disp_delay-1 and BSEL_CNT_OUT < total_bytes - 1) then
                next_state <= BSEL;
            end if;
        when BSEL =>
            -- Once the BSEL counter is incremented once, we can go back to the DISP state
            -- so the next byte can be displayed.
            if (rst = '1') then
                next_state <= IDLE;
            else
                next_state <= DISP;
            end if;
    end case;
end process fsm_process;

-- We want the display delay counter to be reset only when the state turns IDLE or BSEL
DISP_CNT_RST <= '1' when state = IDLE or state = BSEL else
    '0';

-- The byte select counter needs to be reset only at IDLE state.
BSEL_CNT_RST <= '1' when state = IDLE else
    '0';

-- The display delay counter needs to be enabled at the DISP state so the logic can hold
-- the LED display so it's visible to the user.
DISP_CNT_EN <= '1' when state = DISP else
    '0';

-- The byte select counter needs to be enabled only at the BSEL state so the counter can
-- increment so that the DISP state logic can use the counter value as an index for which

```

```

-- byte to display.
BSEL_CNT_EN <= '1' when state = BSEL else
    '0';

-- Once the DISP state has been reached with the delay and byte select counter at zero,
-- the data source needs to be enabled so the next value can be computed and displayed.
EN_SOURCE <= '1' when state = DISP and DISP_CNT_OUT = 0 and BSEL_CNT_OUT = 0 else
    '0';

-- The correct byte needs to be displayed via the LED display. In the DISP state, the BSEL
-- counter is used as an index and the bytes are displayed.
LED_DISPLAY <= SOURCE_DATA(31 downto 24) when state = DISP and BSEL_CNT_OUT = 0 else
    SOURCE_DATA(23 downto 16) when state = DISP and BSEL_CNT_OUT = 1 else
    SOURCE_DATA(15 downto 8) when state = DISP and BSEL_CNT_OUT = 2 else
    SOURCE_DATA(7 downto 0) when state = DISP and BSEL_CNT_OUT = 3 else
    "00000000";

end Behavioral;

```

### 3 - VHDL Testbench

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

ENTITY TOP_LEVEL_tb IS
END TOP_LEVEL_tb;

-- TEST STRATEGY
--
-- Global Reset & Initialisation:
--   Outside of this vector, all btn inputs will initialise
--   to zeros, followed by a reset button click.
--
-- TEST 1:
--   Cycle through the first 5 values, this is to ensure that
--   all logic within this circuit is functioning properly.
--
-- TEST 2:
--   Following from TEST 1, a reset will be inputted via the
--   pushbutton. This is to verify that the circuit resets
--   properly and goes back to the initial state.
--
-- TEST 3:
--   Cycle through the first 5 values just like in TEST 1, but
--   the enable button will be pressed while the FSM is in the
--   DISP state (after the 2nd input). This test will verify
--   that the enable input will be ignored when the FSM is not
--   in IDLE state.
--
-- TEST 4:
--   Continue from TEST 3, the reset button will be toggled after
--   the 4th input, this will verify that the circuit can be reset
--   while the FSM is in operation.
ARCHITECTURE behavior OF TOP_LEVEL_tb IS
    --Inputs
    signal GCLK : STD_LOGIC;
    signal BTN : STD_LOGIC_VECTOR(4 downto 0);
    signal SW : STD_LOGIC_VECTOR(7 downto 0);

```

```

--Outputs
signal LED : STD_LOGIC_VECTOR(7 downto 0);
-- Clock period definitions
constant GCLK_period : time := 10 ns;
-- Defining a record of valid outputs to verify the circuit.
-- The inputs to this circuit (via pushbuttons) will be done
-- outside of the test vector array.
type valid_output_array is array (natural range <>) of STD_LOGIC_VECTOR(7 downto 0);
constant valid_outputs : valid_output_array := (
    -- OUTPUT 1 (4800C00B)
    (X"48"),
    (X"00"),
    (X"C0"),
    (X"0B"),
    -- OUTPUT 2 (0000CA5F)
    (X"00"),
    (X"00"),
    (X"CA"),
    (X"5F"),
    -- OUTPUT 3 (0000570E)
    (X"00"),
    (X"00"),
    (X"57"),
    (X"0E"),
    -- OUTPUT 4 (0380DFAD)
    (X"03"),
    (X"80"),
    (X"DF"),
    (X"AD"),
    -- OUTPUT 5 (0000006C)
    (X"00"),
    (X"00"),
    (X"00"),
    (X"6C")
);
BEGIN
    -- Instantiate the Unit Under Test (UUT)
    uut: entity work.TOP_LEVEL
    GENERIC MAP (disp_delay => 30)
    PORT MAP (
        GCLK => GCLK,
        BTN => BTN,
        SW => SW,
        LED => LED
    );

    -- Clock process definitions
    GCLK_process : process
    begin
        GCLK <= '0';
        wait for GCLK_period/2;
        GCLK <= '1';
        wait for GCLK_period/2;
    end process;

    -- Stimulus process
    set_inputs : process
    begin
        -- hold reset state for 100 ns.
        wait for 100 ns;

```

```

-- TEST 1:
-- Global Reset & Initialisation
-- Duration: 24 clock cycles
BTN <= "00000";
SW <= "00000000";
wait for GCLK_period*18;
BTN(1) <= '1';
wait for GCLK_period*6;
BTN(1) <= '0';

wait for GCLK_period*18;

-- TEST 1
-- Duration:
-- 5 vectors * (132 clk cycles)
-- 660 clock cycles
test_1_loop : for i in 0 to 4 loop
    BTN(3) <= '1';
    wait for GCLK_period*6;
    BTN(3) <= '0';
    -- We need to wait for 124 clock cycles as we need to
    -- account for 4x DISP (30 clk cycles) + 3x BSEL (1 clk cycle)
    -- plus 3 clock cycles for the IDLE state
    wait for GCLK_period*126;
end loop;

-- TEST 2
-- Duration: 6 clock period
BTN(1) <= '1';
wait for GCLK_period*6;
BTN(1) <= '0';

wait for GCLK_period*18;

-- TEST 3
-- Duration:
-- 5 vectors * (132 clk cycles)
-- 660 clock cycles
test_3_loop : for i in 0 to 3 loop
    BTN(3) <= '1';
    wait for GCLK_period*6;
    BTN(3) <= '0';

    -- Toggle enable after the 2nd vector has been passed.
    if (i = 1) then
        wait for GCLK_period*25;
        BTN(3) <= '1';
        wait for GCLK_period*6;
        BTN(3) <= '0';
        wait for GCLK_period*95;
    elsif (i /= 3) then
        -- We need to wait for 124 clock cycles as we need to
        -- account for 4x DISP (30 clk cycles) + 3x BSEL (1 clk cycle)
        -- plus 3 clock cycles for the IDLE state
        wait for GCLK_period*126;
    end if;
end loop;

-- TEST 4
-- Duration: 31 clock period
wait for GCLK_period*25;

```



```

    BTN(1) <= '1';
    wait for GCLK_period*6;
    BTN(1) <= '0';

    wait for GCLK_period*18;

    wait;
end process;

check_outputs : process
begin
    -- Wait for hold reset state.
    wait for 100 ns;
    -- Wait for Global Reset & Initialisation
    wait for GCLK_period*42;

    -- TEST 1
    test_1_test_check_loop : for i in 0 to 19 loop
        -- Wait for the enable signal to toggle
        wait for GCLK_period*6;
        -- Check if the LED output matches the array of known valid output at
        -- the end of every enable btn toggle, as soon as the btn is depressed.
        -- Notify if it's a pass or fail. I'm using severity warning to ensure
        -- that the simulation doesn't halt as soon as a vector fails like it
        -- does for severity failure.
        assert (( LED = valid_outputs(i) ))
        report "TEST VECTOR " & integer'image(i) &
            " FAIL. Observed LED Output = " & integer'image(to_integer(unsigned(LED))) &
            " Expected LED Output = " & integer'image(to_integer(unsigned(valid_outputs(i))))
        severity warning;
        report "TEST VECTOR " & integer'image(i) & " PASS."
        severity note;
        wait for GCLK_period*25;
        -- Wait for an additional 8 clk periods at the end of the 4 LED bytes
        -- display to synchronise with the next input.
        if ( (i+1) mod 4 = 0 ) then
            wait for GCLK_period*8;
        end if;
    end loop;

    -- TEST 2
    -- wait for 6 clk periods for the push button to finish toggling
    wait for GCLK_period*6;
    assert (( LED = X"00" ))
    report "TEST 2 " &
        " FAIL. Observed LED Output = " & integer'image(to_integer(unsigned(LED))) &
        " Expected LED Output = 0"
    severity warning;
    report "TEST 2 PASS."
    severity note;

    wait for GCLK_period*18;

```


```
-- TEST 3
test_3_test_check_loop : for i in 0 to 11 loop
    -- Wait for the enable signal to toggle
    wait for GCLK_period*6;
    -- Check if the LED output matches the array of known valid output at
    -- the end of every enable btn toggle, as soon as the btn is depressed.
    -- Notify if it's a pass or fail. I'm using severity warning to ensure
    -- that the simulation doesn't halt as soon as a vector fails like it
    -- does for severity failure.
    assert (( LED = valid_outputs(i) ))
    report "TEST VECTOR " & integer'image(i) &
        " FAIL. Observed LED Output = " & integer'image(to_integer(unsigned(LED))) &
        " Expected LED Output = " & integer'image(to_integer(unsigned(valid_outputs(i))))
    severity warning;
    report "TEST VECTOR " & integer'image(i) & " PASS."
    severity note;
    wait for GCLK_period*25;
    -- Wait for an additional 8 clk periods at the end of the 4 LED bytes
    -- display to synchronise with the next input.
    if ( (i+1) mod 4 = 0 ) then
        wait for GCLK_period*8;
    end if;
end loop;

-- TEST 4
-- wait for 6 clk periods for the push button to finish toggling
wait for GCLK_period*6;
-- wait for reset to be toggled
wait for GCLK_period*31;
assert (( LED = X"00" ))
report "TEST 4 " &
    " FAIL. Observed LED Output = " & integer'image(to_integer(unsigned(LED))) &
    " Expected LED Output = 0"
severity warning;
report "TEST 4 PASS."
severity note;

wait;
end process;
END;
```


## 4 - Behavioural Simulation Waveforms

### Global Reset and Initialisation

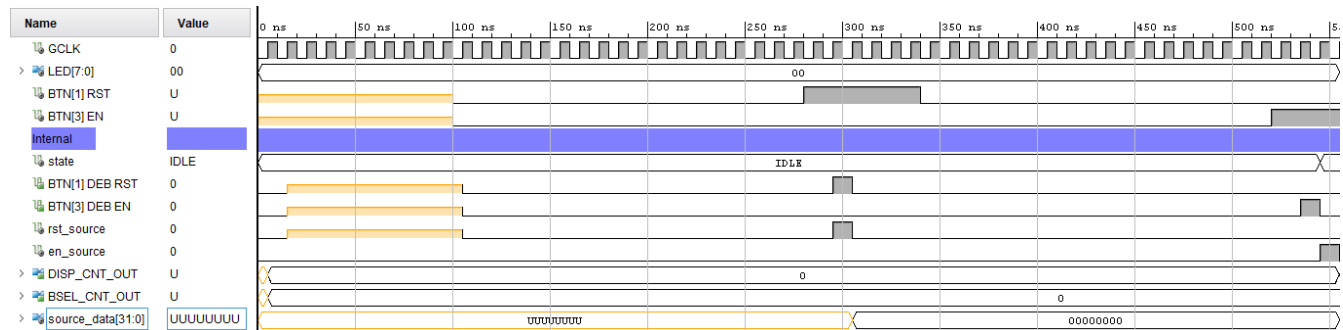


The above waveform shows a global reset, verifying that the circuit can be reset with the 'rst' pushbutton.

### Test 1, Waveform 1

 


The above waveform shows an initial 'en' toggle, followed by the output being computed and the first byte being displayed on the LED, it also verifies that the BSEL counter is fixed with the DISP counting.

### Test 1, Waveform 2

 


This waveform verifies that the DISP counter rolls over correctly, the BSEL increments and the LED is displaying the correct (2nd) byte of the computed output.

## Test 1, Waveform 3

 


This waveform verifies the logic of finishing displaying the 4 bytes with a display delay and setting the next state to IDLE. It also verifies that the 'en' pushbutton can be pressed again to make the logic display the next computed output.

## Test 1, Waveform 4

 


A very zoomed out waveform that verifies the logic as a whole: looking at the first three enable toggles, the correct values are computed, the delays are working perfectly, the byte select is also working as intended with the LEDs displaying the correct output.

## Test 2

 


Following from Test 1, Test 2 consists of a 'rst' toggle to verify that the logic can reset successfully. As the waveform shows, this works as intended.

### Test 3

 

Another very zoomed out waveform which simply verifies that the logic ignores an 'en' toggle when in any state other than IDLE. When the 'en' button is toggled at around 9000ns, the circuit is in DISP and BSEL (shown as the black box due to being zoomed out). The logic successfully ignores it and carries on computing and displaying the next values.

### Test 4

 

This test verifies that the circuit can be reset whilst the FSM is in operation. The logic successfully resets back to the IDLE state with all internal signals and counters reset too. The circuit is now ready to continue operation once the user toggles 'en'.

## 5 - Synthesis Report

### RTL Component Statistics

```
Detailed RTL Component Info :
+---Adders :
      3 Input      32 Bit      Adders := 1
      2 Input      27 Bit      Adders := 1
      2 Input       6 Bit      Adders := 1
      2 Input       2 Bit      Adders := 1
+---Registers :
      32 Bit      Registers := 1
      27 Bit      Registers := 1
      6 Bit       Registers := 1
      2 Bit       Registers := 2
      1 Bit       Registers := 15
+---Muxes :
      2 Input      27 Bit      Muxes := 1
      64 Input     16 Bit      Muxes := 2
      2 Input       6 Bit      Muxes := 1
      2 Input       2 Bit      Muxes := 1
      5 Input       2 Bit      Muxes := 1
      2 Input       1 Bit      Muxes := 5
      4 Input       1 Bit      Muxes := 1
```

### RTL Hierarchical Component Statistics

```
Hierarchical RTL Component report
Module parameterizable_counter
Detailed RTL Component Info :
+---Adders :
      2 Input      27 Bit      Adders := 1
+---Registers :
      27 Bit      Registers := 1
+---Muxes :
      2 Input      27 Bit      Muxes := 1
Module parameterizable_counter__parameterized0
Detailed RTL Component Info :
+---Adders :
      2 Input       2 Bit      Adders := 1
+---Registers :
      2 Bit       Registers := 1
+---Muxes :
      2 Input       2 Bit      Muxes := 1
Module STUDENT_AREA
Detailed RTL Component Info :
+---Registers :
      2 Bit       Registers := 1
+---Muxes :
      5 Input       2 Bit      Muxes := 1
      2 Input       1 Bit      Muxes := 5
      4 Input       1 Bit      Muxes := 1
Module Param_Counter
Detailed RTL Component Info :
+---Adders :
      2 Input       6 Bit      Adders := 1
+---Registers :
      6 Bit       Registers := 1
+---Muxes :
      2 Input       6 Bit      Muxes := 1
```

```
Module MEM_A
Detailed RTL Component Info :
+---Muxes :
      64 Input      16 Bit      Muxes := 1
Module MEM_B
Detailed RTL Component Info :
+---Muxes :
      64 Input      16 Bit      Muxes := 1
Module DATA_SOURCE
Detailed RTL Component Info :
+---Adders :
      3 Input       32 Bit      Adders := 1
+---Registers :
                        32 Bit   Registers := 1
Module Debouncer
Detailed RTL Component Info :
+---Registers :
                        1 Bit    Registers := 3
```